
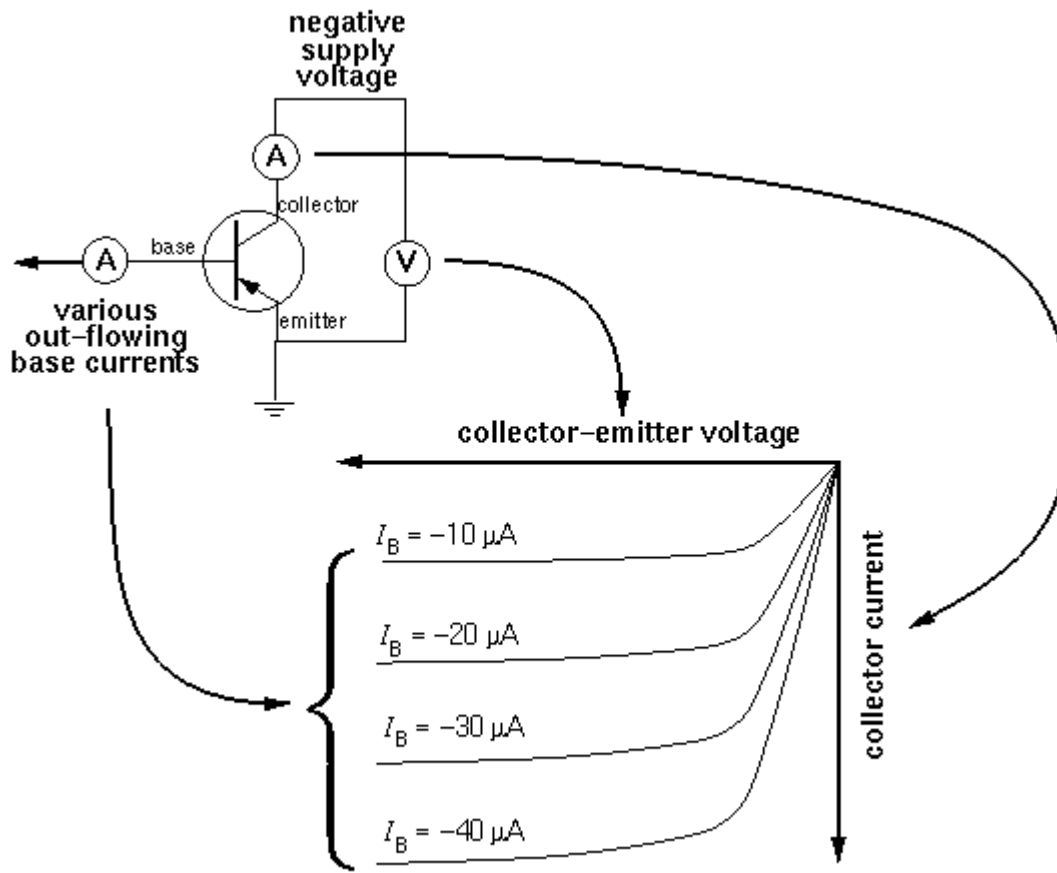


# PNP Characteristic Curves

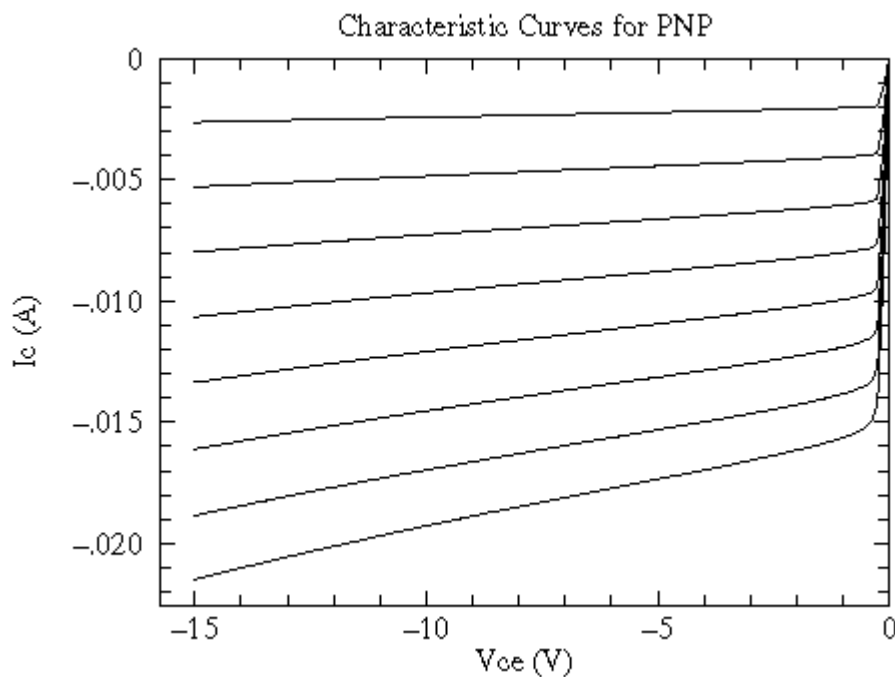


## Measured Characteristic Curves for 2N3906



for  $I_B = -10 \mu\text{A}, -20 \mu\text{A}, -30 \mu\text{A}, \dots, -80 \mu\text{A}$

[big](#) data file, [smaller](#) data file, [postscript](#) plot, [pdf](#) plot

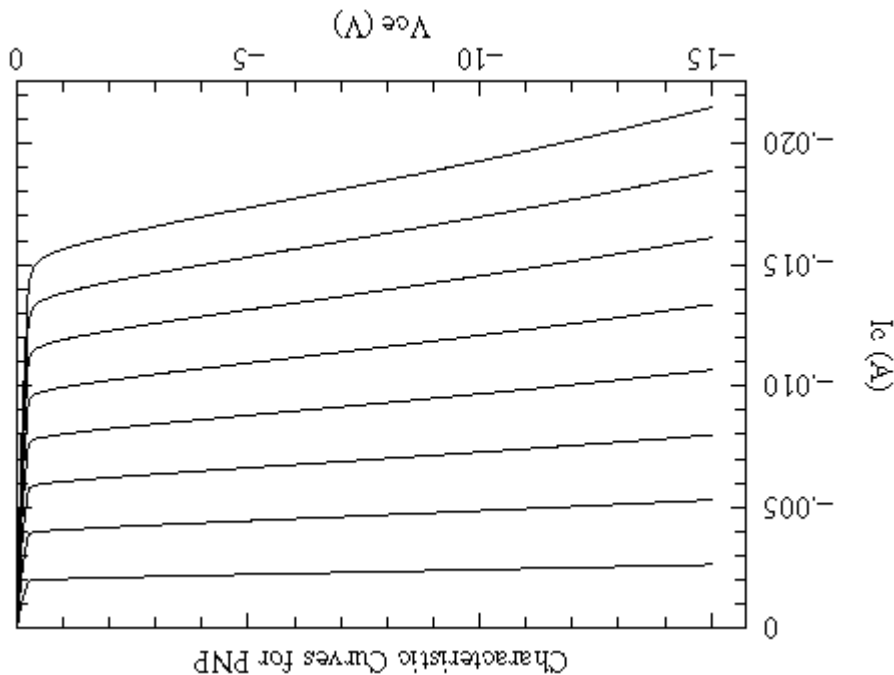Note that you can make the PNP characteristic curves look like the common NPN curves just by rotating the PNP plot by  $180^\circ$ . In swapping N for P so NPN  $\longrightarrow$  PNP, we've reversed the direction of current flows (so currents are negative -- flowing out of the collector and base in a PNP) and the required supply voltage becomes negative for a PNP.




That is to say that the PNP is designed for negative power supplies and out-flowing (negative) base and collector currents -- the opposite of NPNs.

The behavior of a PNP bipolar transistor is largely controlled by the current flowing *out of* the base. For the usual collector-emitter voltage drops (i.e., the active region: negative voltages from a fraction of a volt down to some breakdown voltage) the collector current ( $I_C$ ) is nearly independent of the collector-emitter voltage ( $V_{CE}$ ), and instead depends on the base current ( $I_B$ ). (This is unusual behavior: usually more voltage produces to more current, but here the current only increases slightly with increasingly negative  $V_{CE}$ .) The current gain, i.e., the ratio of the collector current to the base current, is often denoted by  $\beta$  or  $h_{FE}$ :


$$\beta = h_{FE} = I_C / I_B$$

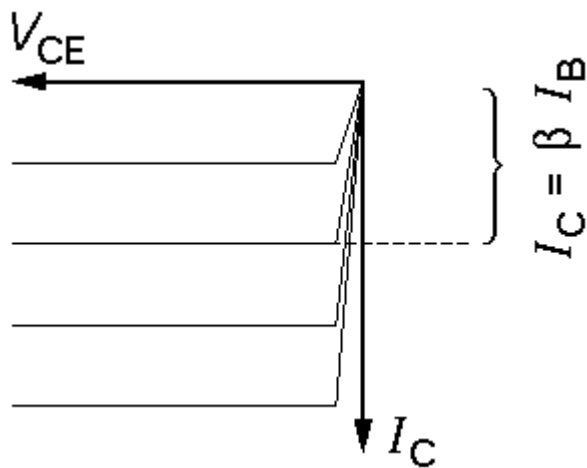Thus in the simplest approximation the characteristic curves of a PNP are a set of flat, evenly spaced, lines:



Each (flat) curve shows that  $I_C$  doesn't change with changing  $V_{CE}$ . The different levels show that  $I_C$  does depend on  $I_B$ .

A slightly more complicated approximation takes into account the sloping characteristic curves through a constant Early Voltage ( $V_A$ ). Here we assume that the characteristic curves all have a common  $x$ -axis intercept at the large positive voltage  $V_A$ . (The dashed curves are far from the active region and in no way represent the actual behavior of the transistor for positive  $V_{CE}$ . In fact, the PNP transistor is not designed to be operated with positive  $V_{CE}$ .)

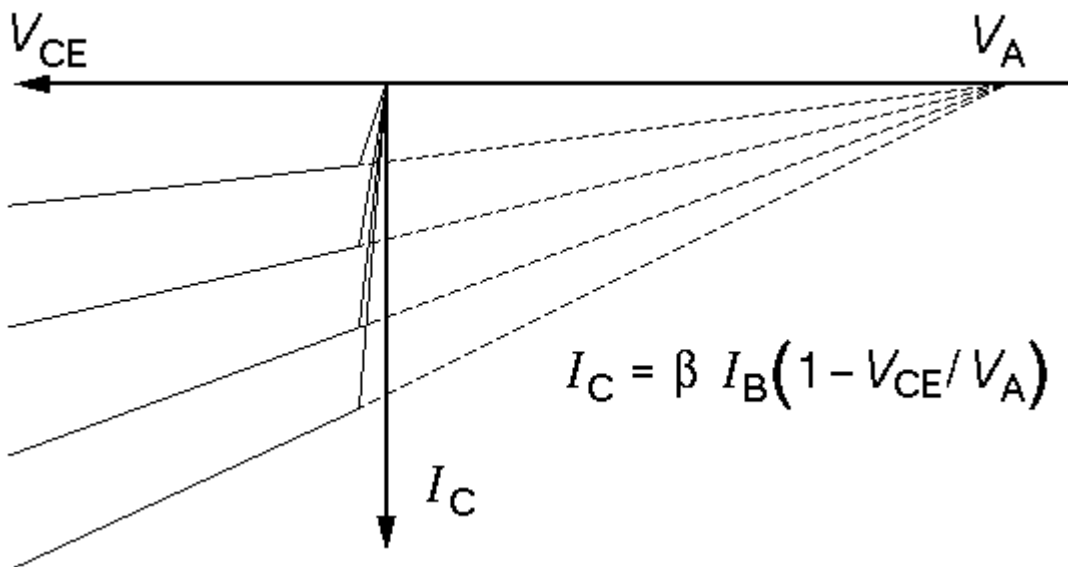

(For the above measured 2N3906, the Early voltage ranges from 40 to 50 V. That is the extrapolated characteristic curves do not intersect at a point.)

The actual relationship between the collector current ( $I_C$ ) and the controlling base current ( $I_B$ ) and collector-emitter voltage drop ( $V_{CE}$ ) is some complicated function which we can denote:

$$I_C(I_B, V_{CE})$$


Like any function we can approximate it near a particular point using just the first terms of a Taylor's expansion:

$$I_C(I_B, V_{CE}) :$$

$$\Delta I_C = h_{fe} \Delta I_B + h_{oe} \Delta V_{CE}$$


$$h_{fe} = \left. \frac{\partial I_C}{\partial I_B} \right|_{V_{CE}=\text{const}} \approx \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{const}}$$

$$h_{oe} = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_{I_B=\text{const}} \approx \left. \frac{\Delta I_C}{\Delta V_{CE}} \right|_{I_B=\text{const}}$$

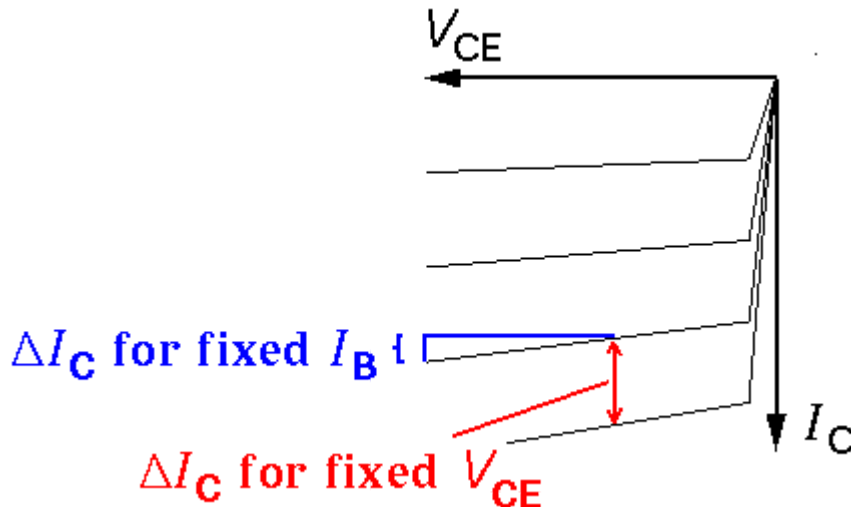

Clearly these *hybrid (h) parameters* are not constants. For example  $h_{oe}$  is the slope of a characteristic curve, which is nearly zero for small  $|I_B|$  and increases for more negative  $I_B$ . (Note that slope on an  $I$ - $V$  is basically the inverse of the resistance. Thus  $1/h_{oe}$  can be described as the output impedance. A typical value for  $1/h_{oe}$  would be 100,000  $\Omega$ .)

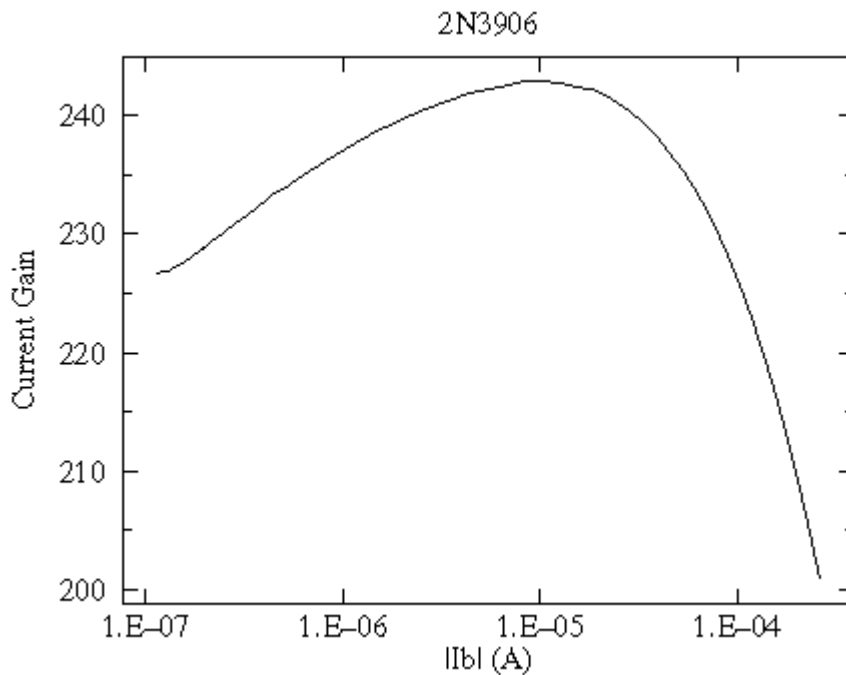Even the defining parameter -- the current gain  $\beta$  or  $h_{FE}$  -- is not exactly constant and depends on  $I_B$ . Here is the measured relationship for the above 2N3906:



The characteristic curves focus on the output of the transistor, but we can also consider the behavior of the input. In the active region the base is a forward biased diode, and so  $V_B$  would be about  $-0.7$  V, typical for a conducting Si diode. Of course in greater detail the relationship between  $V_B$  and  $I_B$  would be given by the Shockley diode equation:

$$I = I_s \left[ \exp \left( \frac{V}{V_T} \right) - 1 \right] \approx I_s e^{V/V_T}$$

where  $I_s$  is a constant and the thermal voltage  $V_T$  is given by:

$$V_T \approx kT/q = \frac{1}{40} V \quad \text{at room temperature}$$

Because of the exponential relationship between base current and base voltage, the slope of this relationship (which could be called the input conductance, or  $1/r_B$ , or  $1/h_{ie}$ ) can be approximated by:

$$\frac{1}{r_B} = \left. \frac{\partial I_B}{\partial V_B} \right|_{V_{CE}=\text{const}} \approx \frac{\partial}{\partial V_B} I_s e^{V_B/V_T} = \frac{1}{V_T} I_s e^{V_B/V_T} = \frac{I_B}{V_T}$$

$$r_B = h_{ie} \approx \frac{V_T}{I_B} = \frac{25 \Omega}{I_B}$$

where in the last equation ( $25 \Omega/I_B$ ) the absolute value of the base current must be entered in mA.

A desirable characteristic of a transistor is that the outputs have little effect on the inputs, but if we look in detail we find that  $V_{CE}$  affects  $V_B$ . The actual functional relationship giving the base voltage from the base current ( $I_B$ ) and collector-emitter voltage drop ( $V_{CE}$ ) is some complicated function which we can denote:

$$V_B(I_B, V_{CE})$$

Like any function we can again approximate it near a particular point using just the first terms of Taylors expansion:

$$V_B(I_B, V_{CE}) :$$

$$\Delta V_B = h_{ie} \Delta I_B + h_{re} \Delta V_{CE}$$

$$h_{ie} = \left. \frac{\partial V_B}{\partial I_B} \right|_{V_{CE}=\text{const}} \approx \frac{V_T}{|I_B|} \approx \frac{25 \Omega}{|I_B|}$$

$$h_{re} = \left. \frac{\partial V_B}{\partial V_{CE}} \right|_{I_B=\text{const}} \sim 10^{-4}$$

The small value of  $h_{re}$  shows that the input is largely unaffected by the output.

The spec sheet reports the following values for the 2N3906:

Characteristics	Symbol	Min	Max	Unit
Input Impedance	$h_{ie}$	2	12	k Ohms
Voltage Feedback Ratio	$h_{re}$	0.1	10	$\times 10^{-4}$
Small-Signal Current Gain	$h_{fe}$	100	400	
Output Admittance	$h_{oe}$	3.0	60	$\mu\text{ mhos}$